


Additional Useful Materials...

Prof. Greg Kovacs

Department of Electrical Engineering

Stanford University

Simple D/A Converter

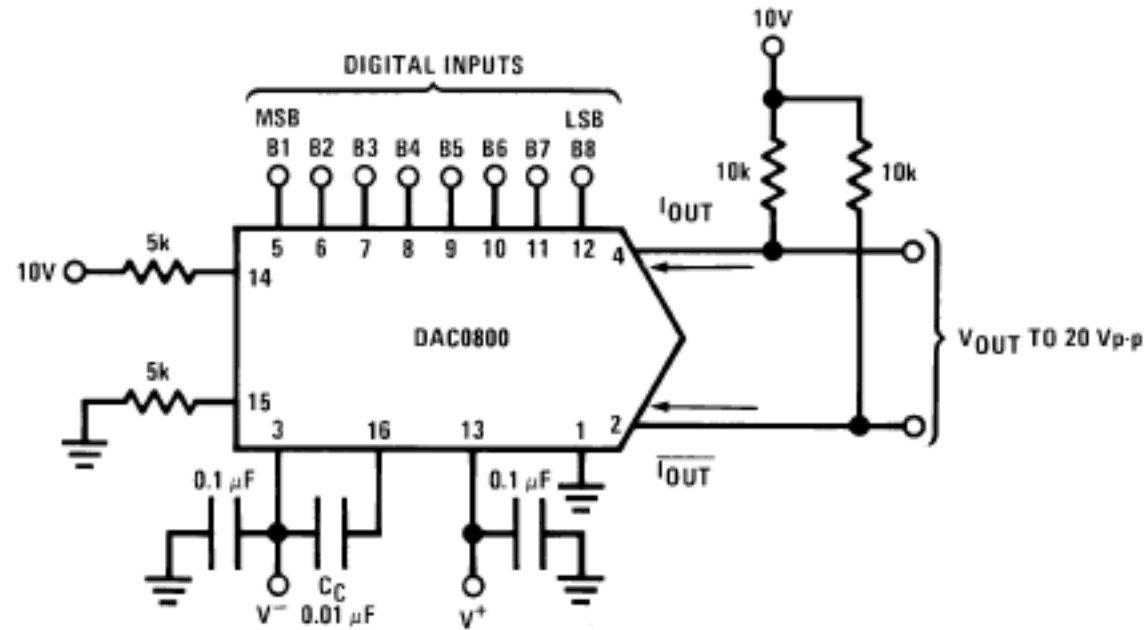

DS005686-1

FIGURE 1. ± 20 V_{P-P} Output Digital-to-Analog Converter (Note 5)

Source: National Semiconductor DAC0800 datasheet.



All About Switches

- Switches are available in a wide variety of types.
- Normally, they are identified by the number of contacts and the number of positions, or “throws” for each contact. The most popular:


– SPST = single-pole, single-throw



– SPDT = single-pole, double-throw




– DPDT = double-pole, double-throw

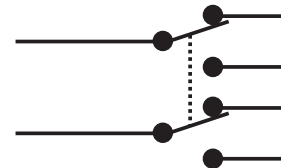


- Switches are also either latching or momentary.
- Current and voltage ratings are important if significant power is to be controlled.





Example Switches

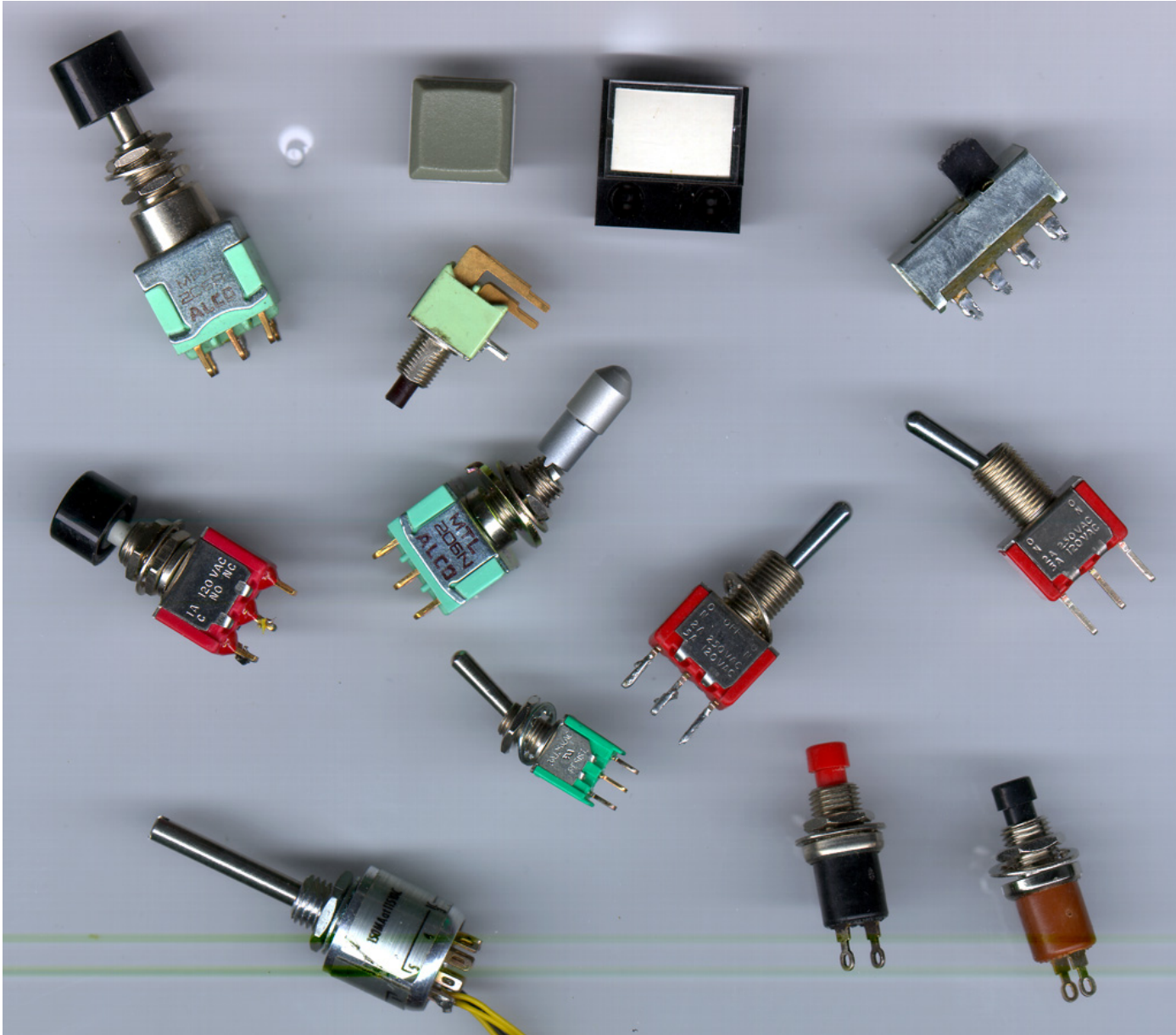


Typical DPDT Connections

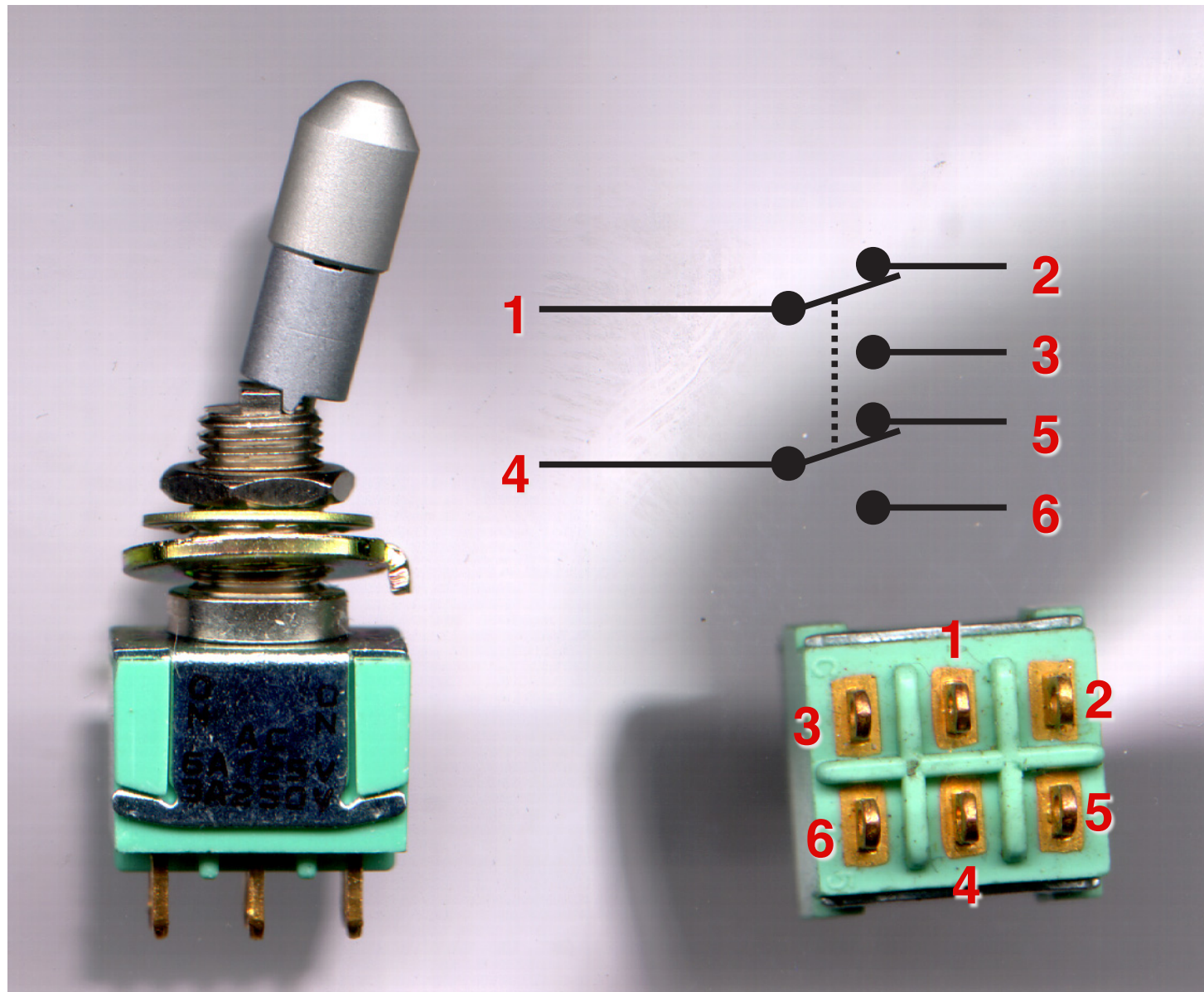

Switch Bounce

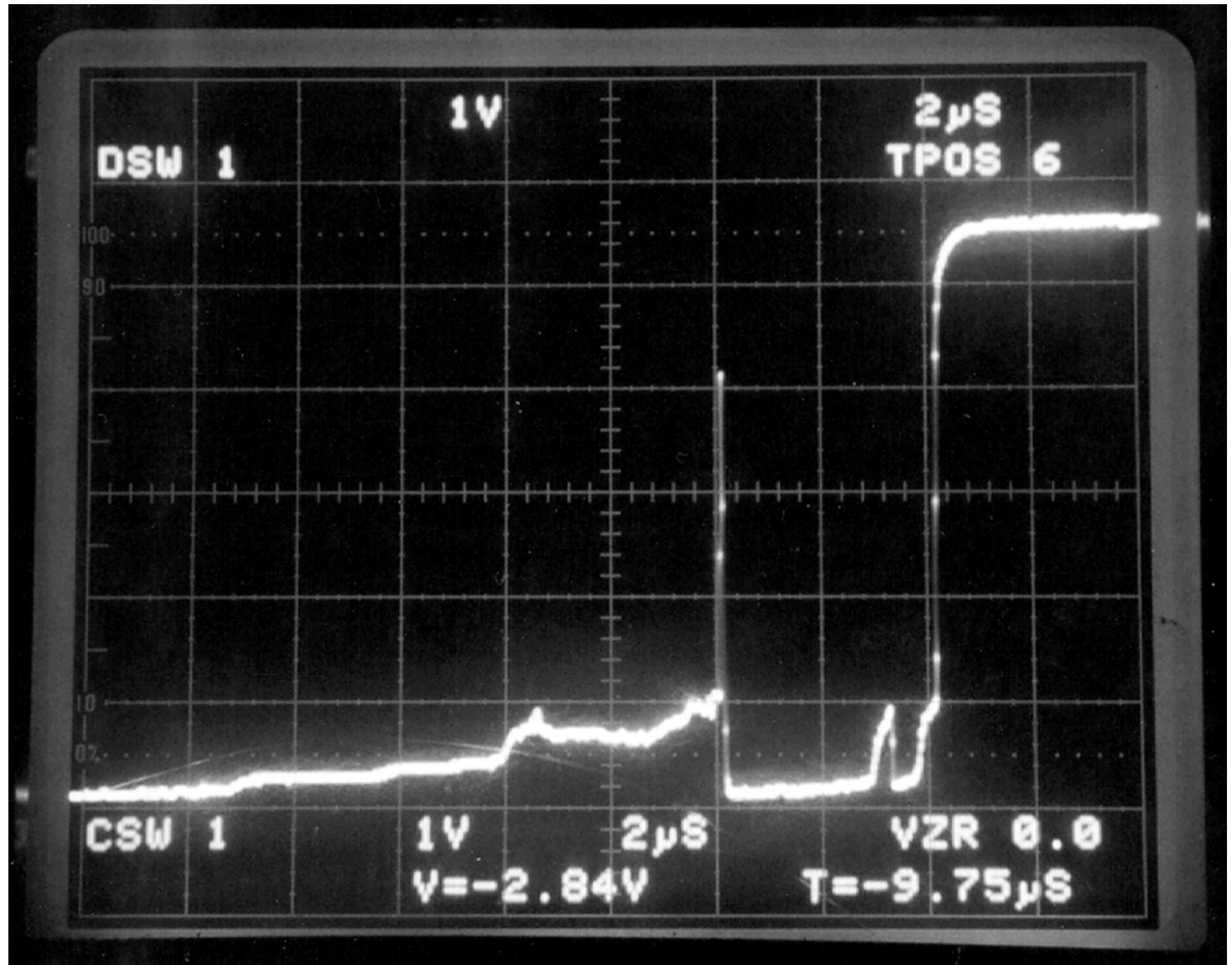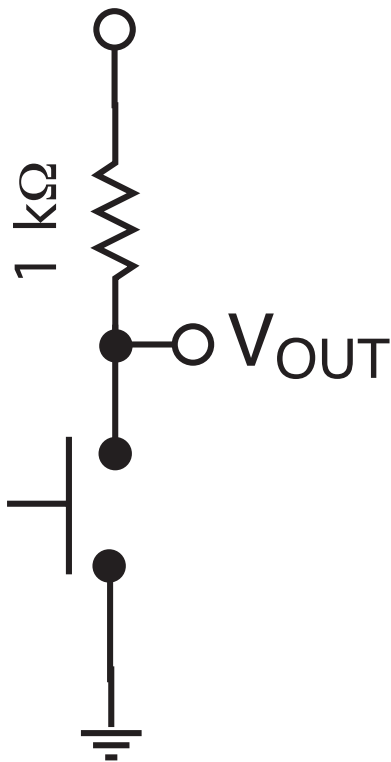

A Debounce Strategy

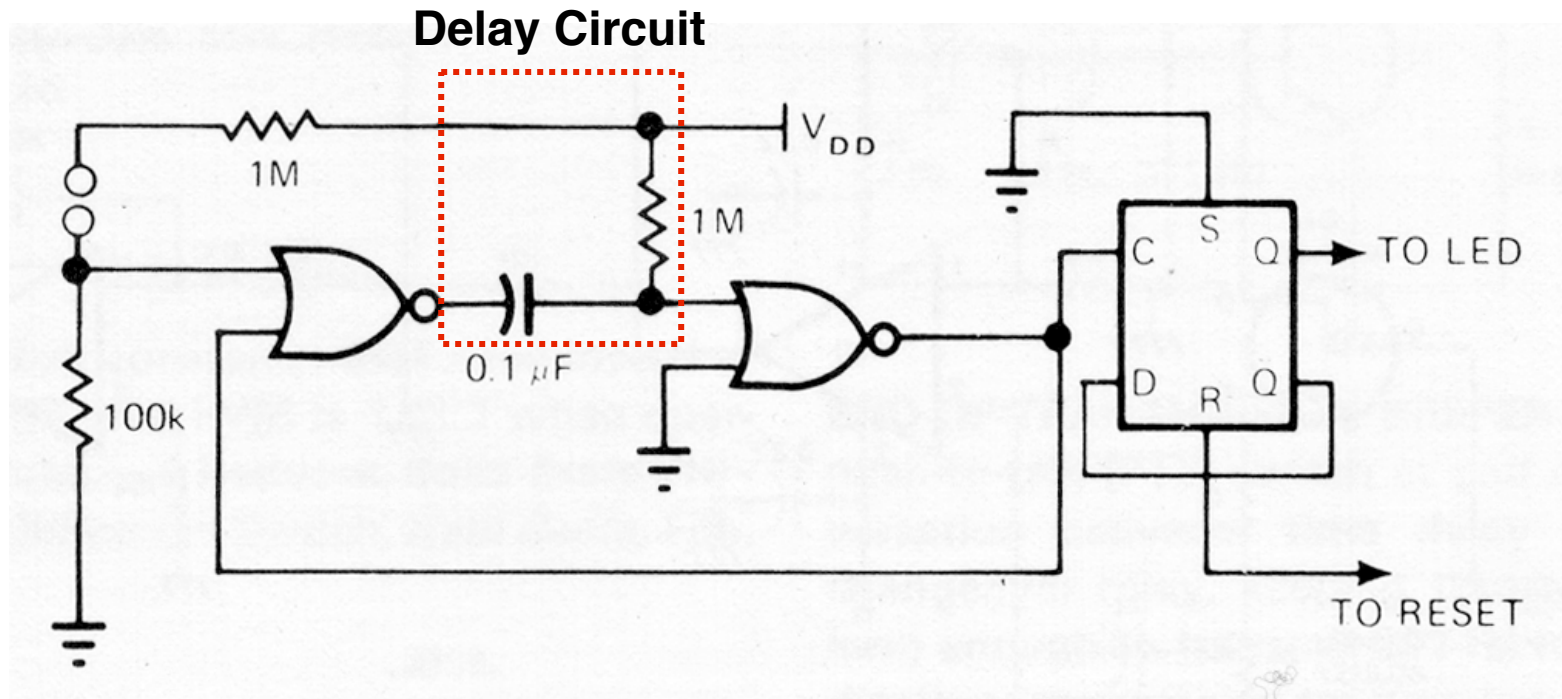


**Works with a conventional pushbutton switch
or as a touch switch.**

Source: V. Gregory, EDN Magazine, May 5, 1976, p. 112



Another Debounce Strategy

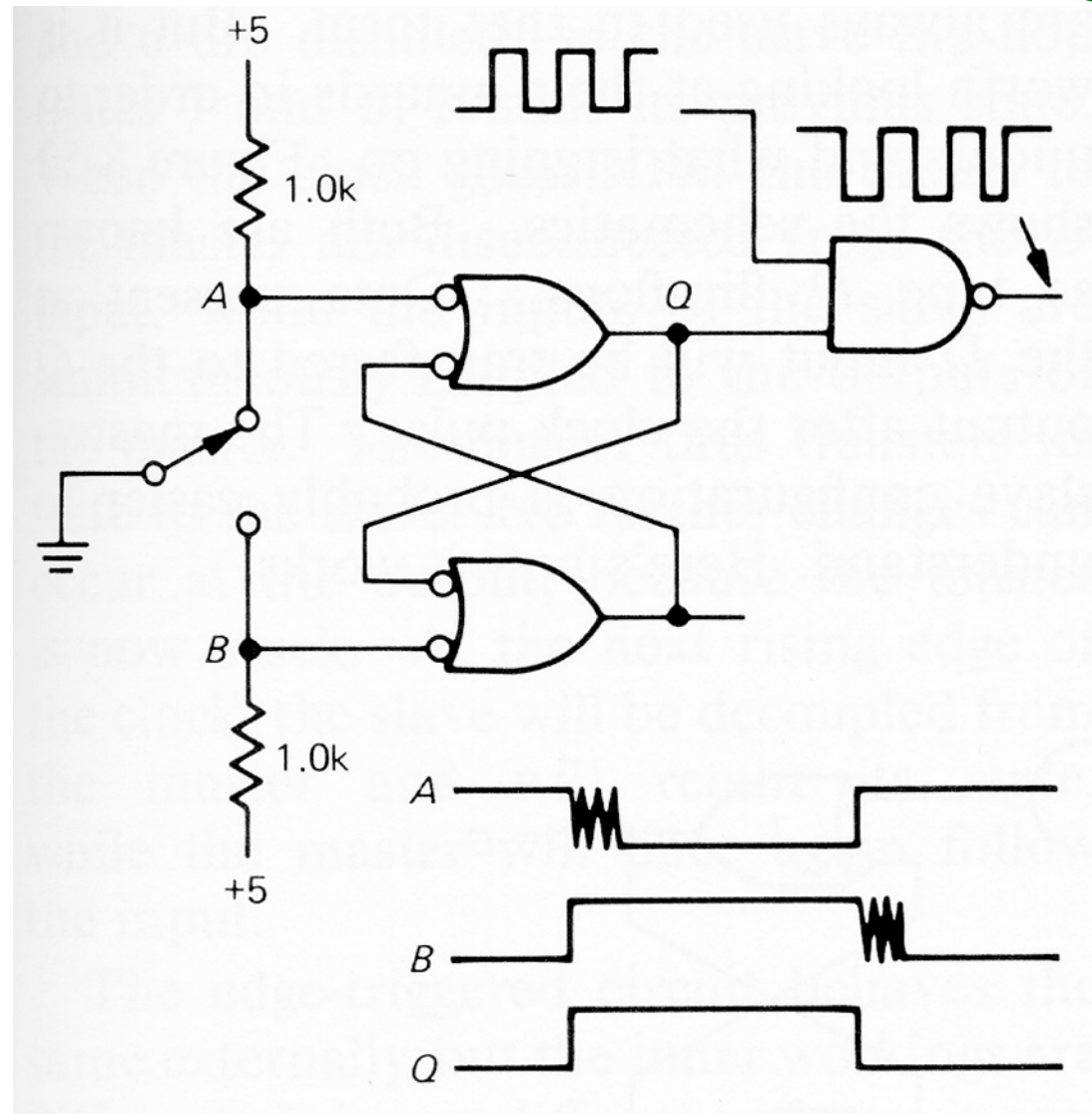

Source: Horowitz & Hill, Second Edition, Cambridge University Press, 1989.
EE122A, Stanford University Copyright © 2020, Prof. Greg Kovacs

Commercial Debounce Chips

- There are commercially available integrated circuits specifically designed for switch debouncing.
- A good example is the Maxim 6816 and related chips, which interface directly between mechanical switches and logic circuits.
- The MAX6816 is a one-switch unit in a tiny 4-pin SOT-23 package, and the 6817 is a two-switch unit in a 6-pin SOT-23.
- The MAX6818 handles eight switches and provides a signal if any are pressed (can be used to interrupt a microprocessor or load a latch, for example.)



Outstanding Cubicle Prank of 2000






Another Type of Switch



Touch Switch That Uses Noise

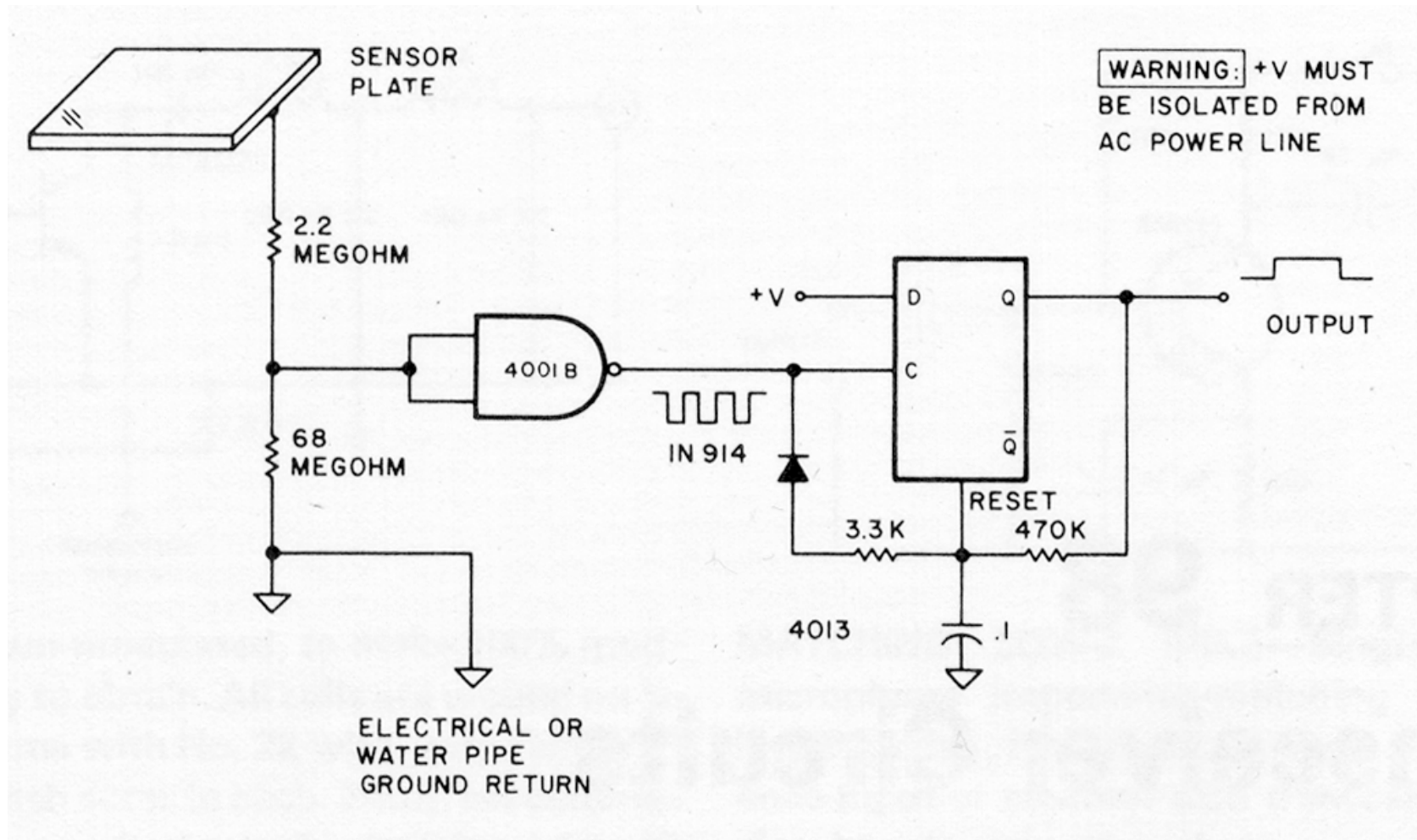


Source: D. Lancaster, Clocked Logic, Kilobaud Magazine, May 1977, pp. 24 - 30.



What Was Marketing Thinking?




Design Idea: PLL Phase Shifter

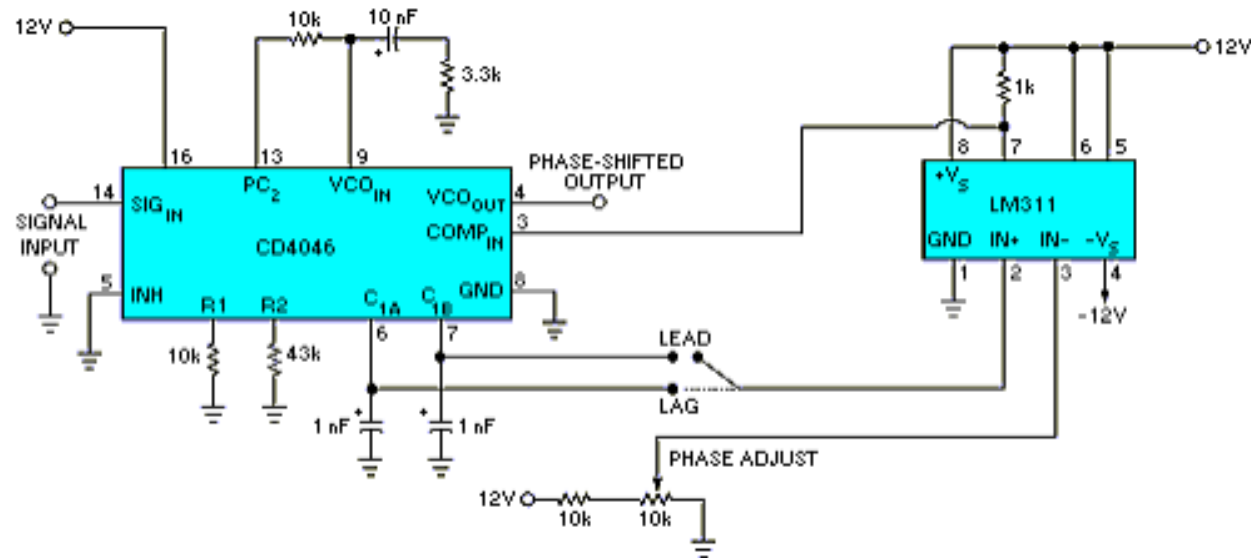

Source: H. Karaca,
EDN Magazine.



Design Idea: 10-Octave Audio Generator

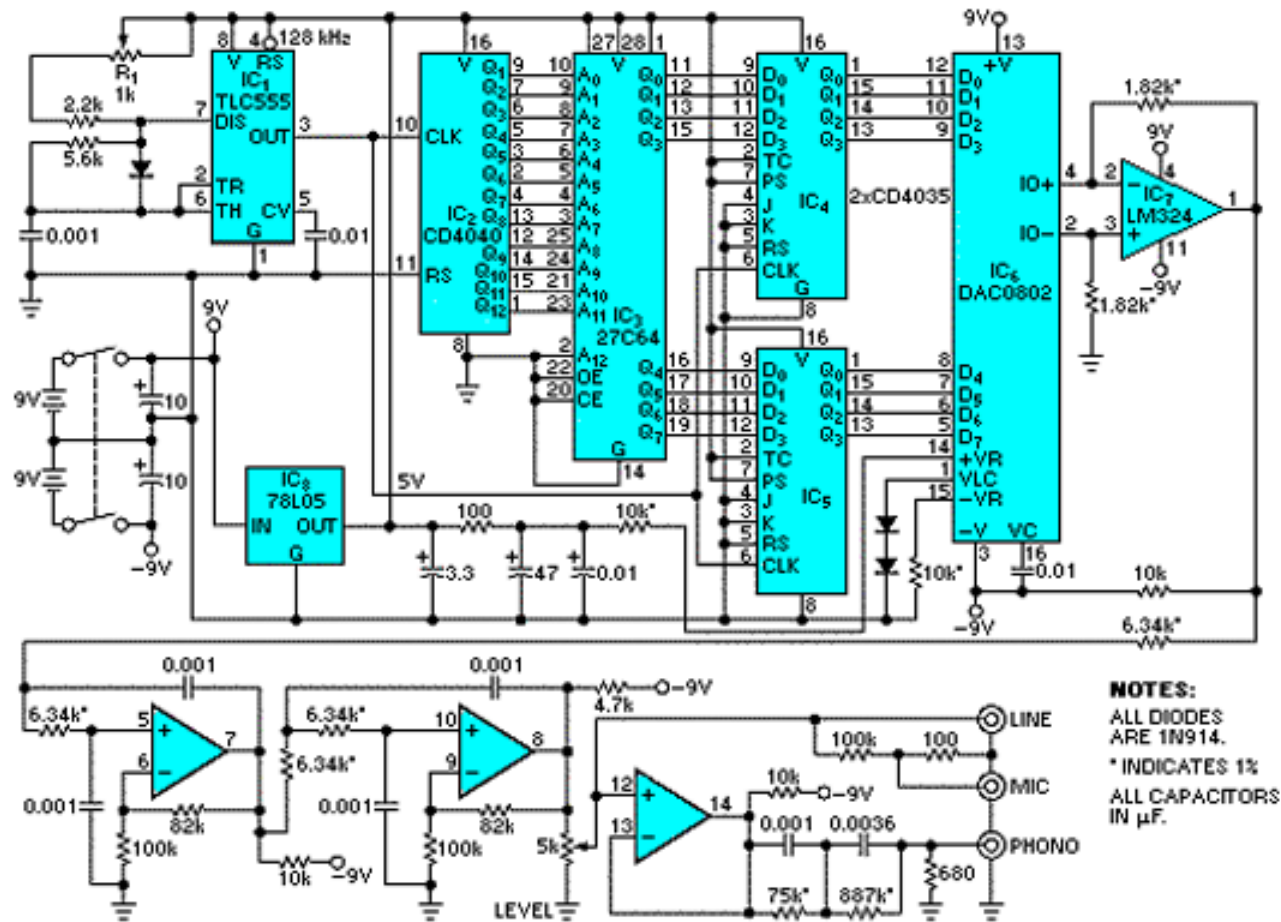

Source: W. Sward,
 EDN Magazine.






Contributed by: Gene Berdichevsky, Fall 03/04



Design Idea: Novel Peltier Controller

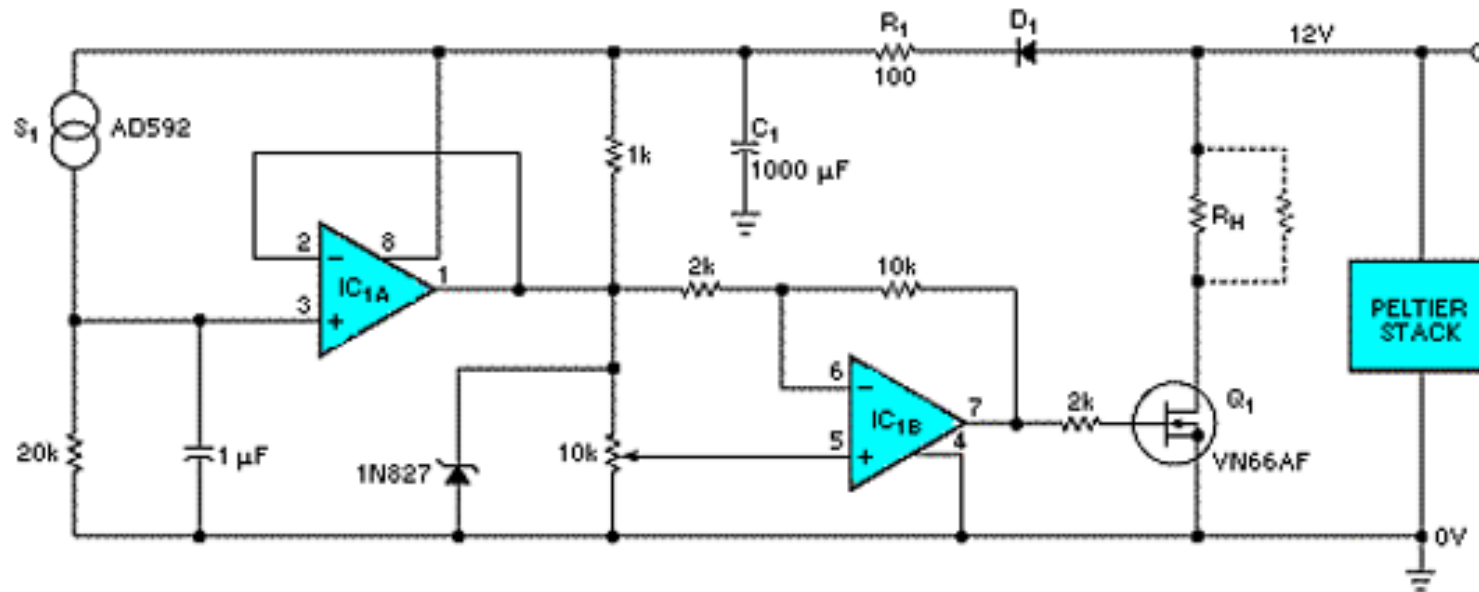

Source: T. Preston,
EDN Magazine.




Electroluminescent Lamps



- Low-cost, flexible devices for generating light (common as LCD backlights).
- Circuit model: leaky capacitor ($\approx 3 - 6 \text{ pF/in}^2$ with a parallel resistance of $\approx 50\text{k} - 1.5\text{M}\Omega/\text{in}^2$).
- Usually driven at 120 VRMS and 400 Hz.
- Many drive circuits and chips exist



EL Lamp Structure

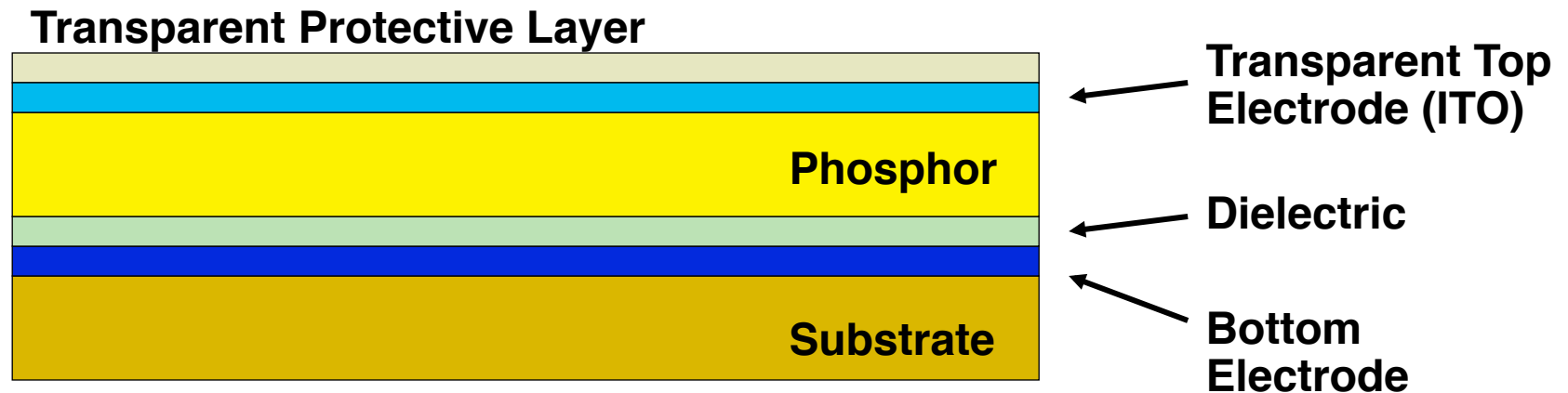

EL Lamp/Chip Sources

EL LAMPS

- Durel Corp. (602) 917-6000, www.durel.com
- MetroMark, Inc. (800) 680-5556, www.metromark.com
- LSI (603) 448-3444, www.metromark.com

CHIPS

- Durel (as above)
- IMP, Inc. (408) 744-0100, www.impweb.com
- Sipex Corp. (978) 667-8700, www.sipex.com
- Supertex, Inc. (408) 744-0100, www.supertex.com



Last Year's Toys = Tomorrow's Hack!

